

VOLTAGE MODE CONTROL FOR BUCK BOOST CONVERTER

CHANDAN KUMAR 2023EEM1044
AMIT KUMAR 2023EEM1039

OBJECTIVE:---

- ① 1. Simulate a closed loop buck-boost converter with voltage mode control
- ② 2. Obtain the bode plot before and after the controller design and show that a phase margin of 50 degrees is achieved.
- ③ 3. Draw the nyquist plot of open loop gain and confirm the same as in 2
- ④ 4. Draw the root-locus of the output capacitor series resistance variation and show the limits of the capacitor series resistance variation for stable operation.

Parameters used:----

- ◉ $V_{in}=14$ Volts
- ◉ $V_o= 30$ Volts
- ◉ $L_{in}=10$ mH
- ◉ $C=480$ μ F
- ◉ $R=3.2\Omega$
- ◉ $f=40$ KHZ
- ◉ $\Delta I=2\%$

Transfer function for voltage mode control

- Open loop transfer function without controller

$$GH(s) \frac{V_c}{d} = \frac{\frac{(1-D)(V_{dc}+V_c)}{LC} - \frac{sI_1}{C}}{s^2 + \frac{s}{RC} + \frac{(1-D)^2}{LC}}$$


Gp =

-4.34e04 s + 5.062e06

s^2 + 651 s + 4.126e04

Bode Diagram

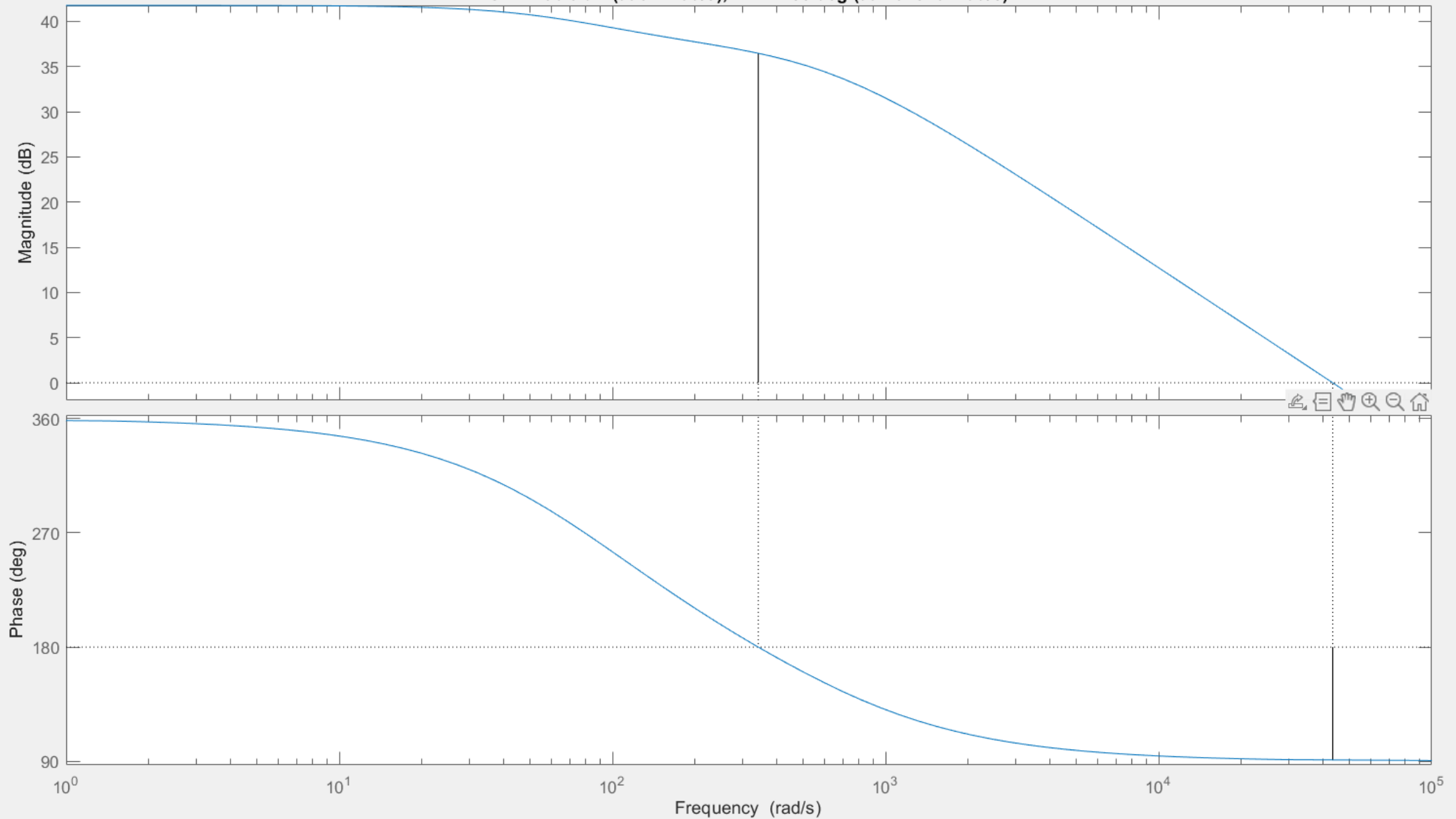Gm = -36.5 dB (at 342 rad/s), Pm = -89 deg (at 4.34e+04 rad/s)



Open loop transfer function with controller

$$\blacktriangleright GH(s) = \frac{\frac{(1-D)(V_{dc}+V_c)}{LC} - \frac{sI_L}{C}(K_p + \frac{K_i}{s})}{s^2 + \frac{s}{RC} + \frac{(1-D)^2}{LC}}$$


$$\odot G(s)H(s) = \frac{(K_p * 43402.833) * (116.64 - s)(s + K_p/K_i)}{s(s + 71.147)(s + 579.85)}$$

By using dominant pole concept, we take $K_p/K_i = 71.147$

PI coefficient used in controller

- ◉ We take K_p value such such that our DC gain will be small.
- ◉ $K_p = 0.005$
- ◉ $K_i = 0.471$

Simulation model:-

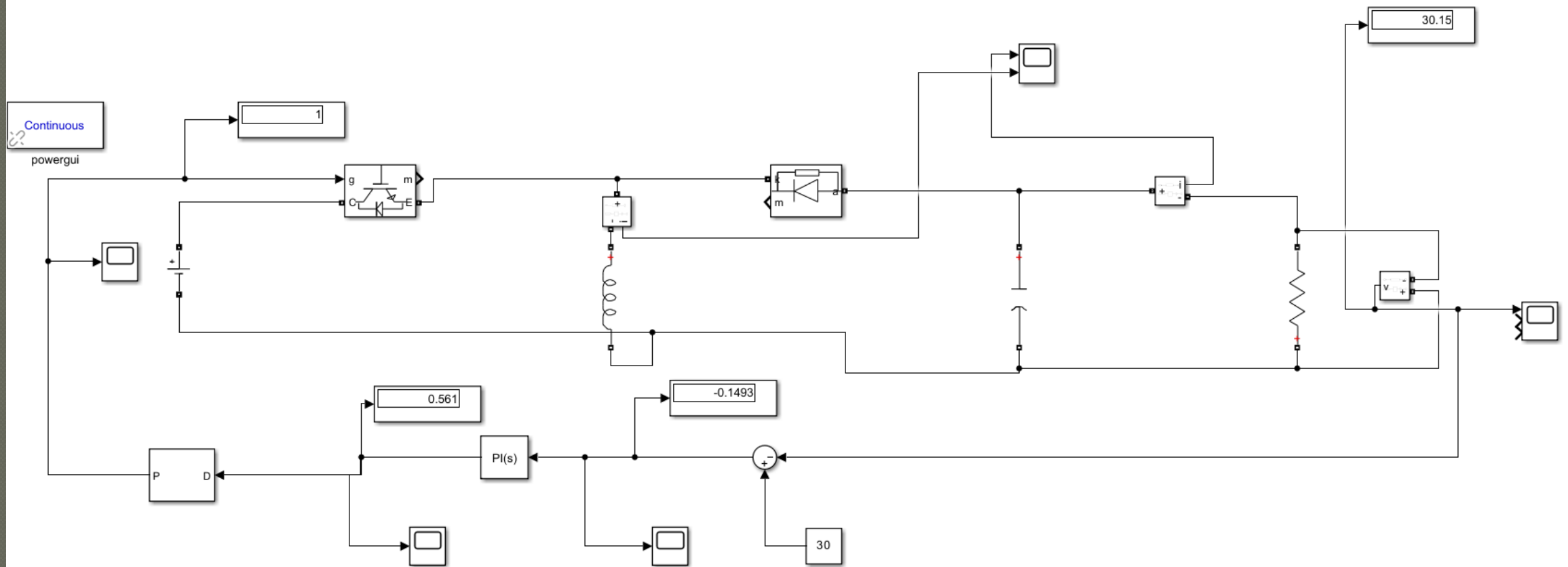

Vout waveform:-




overshoot(for $k=0.009$):-



Bode plot without controller:-

Gp =
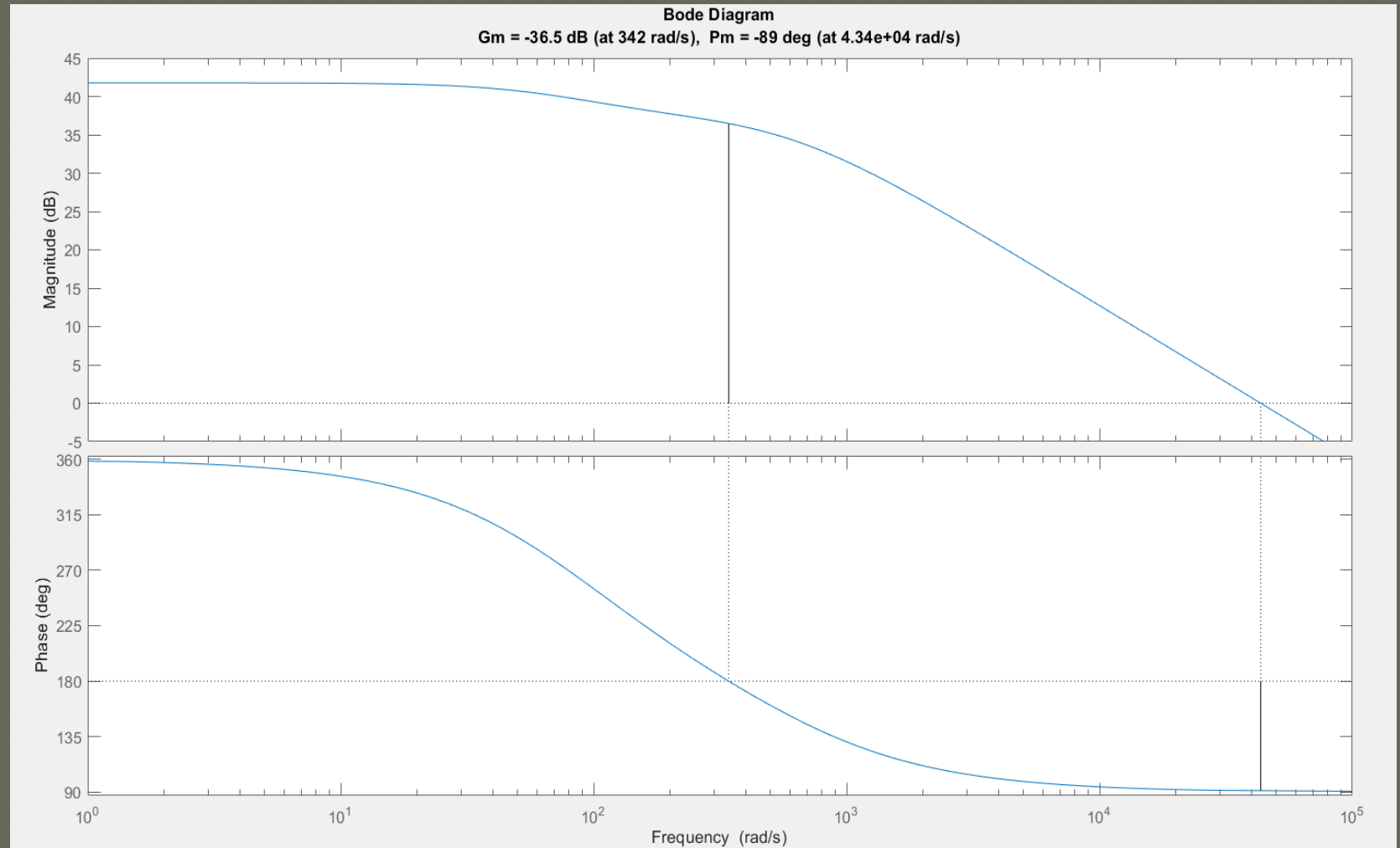
$$\frac{-4.34e04 s + 5.062e06}{s^2 + 651 s + 4.126e04}$$




Bode plot with controller:-


G =

$$\frac{-217 s^2 + 4869 s + 2.384e06}{s^3 + 651 s^2 + 4.126e04 s}$$

Continuous-time transfer function.

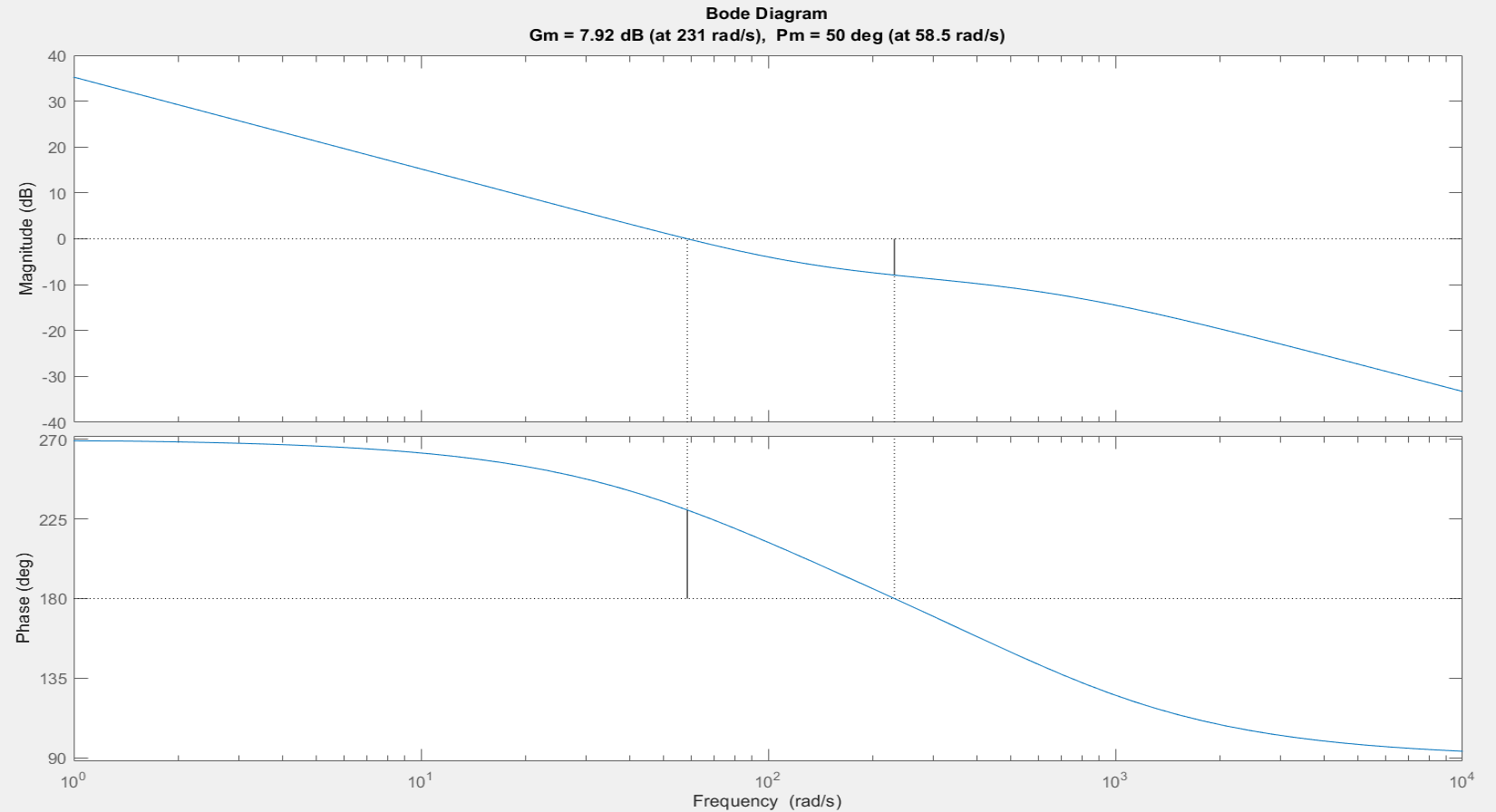


Nyquist plot without controller:-

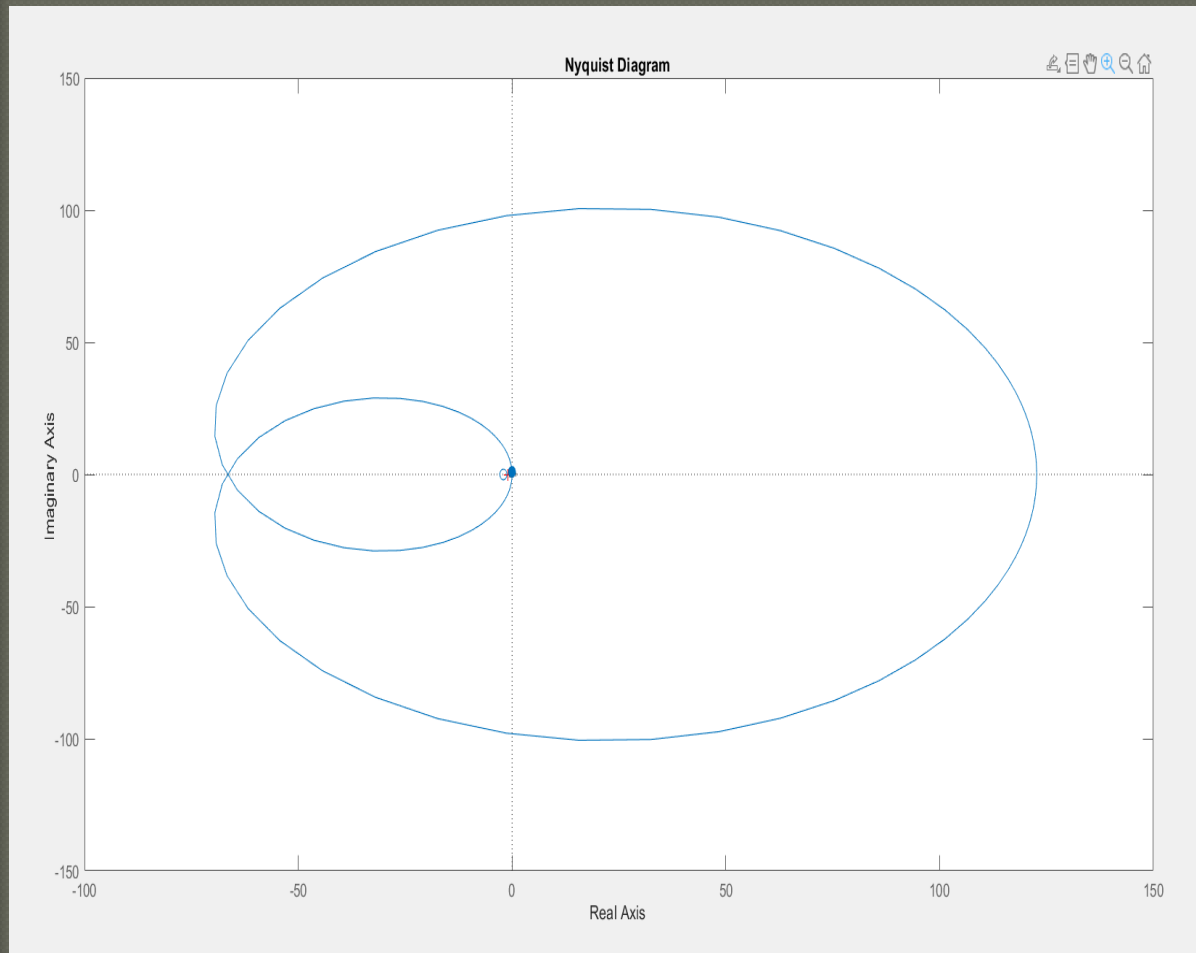


ans =

-579.8522

-71.1478

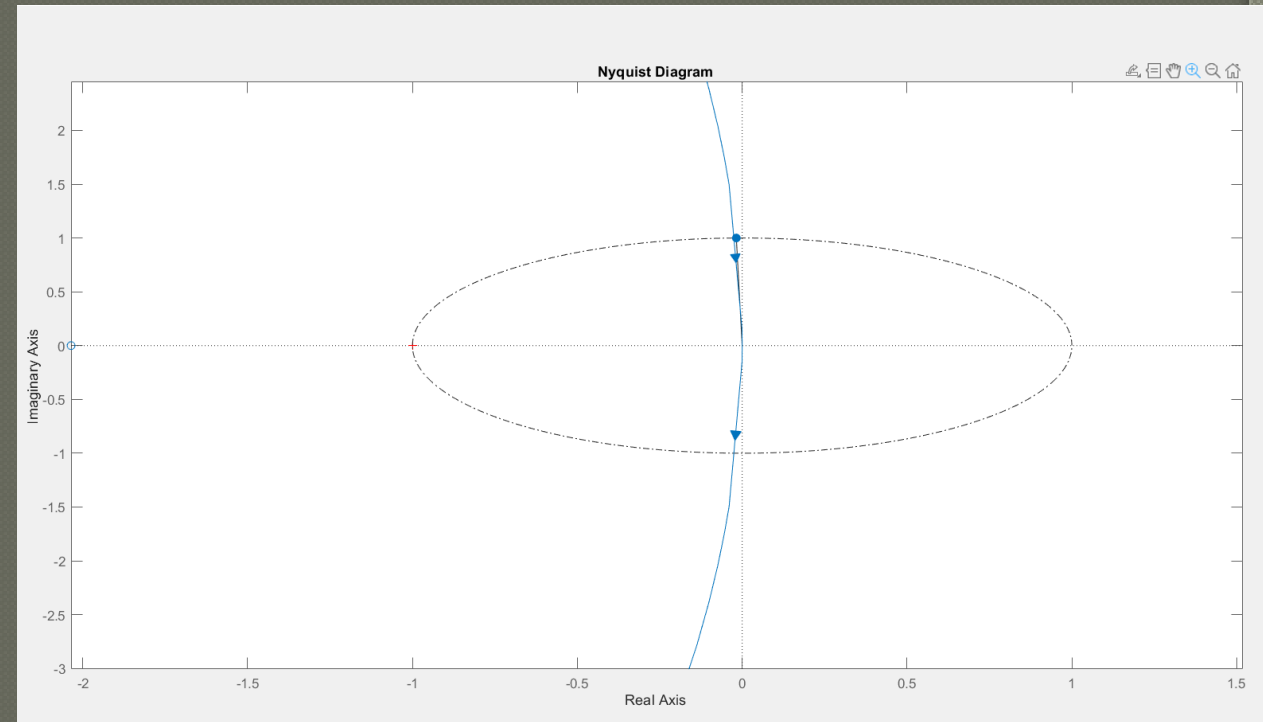


Nyquist plot with controller:-

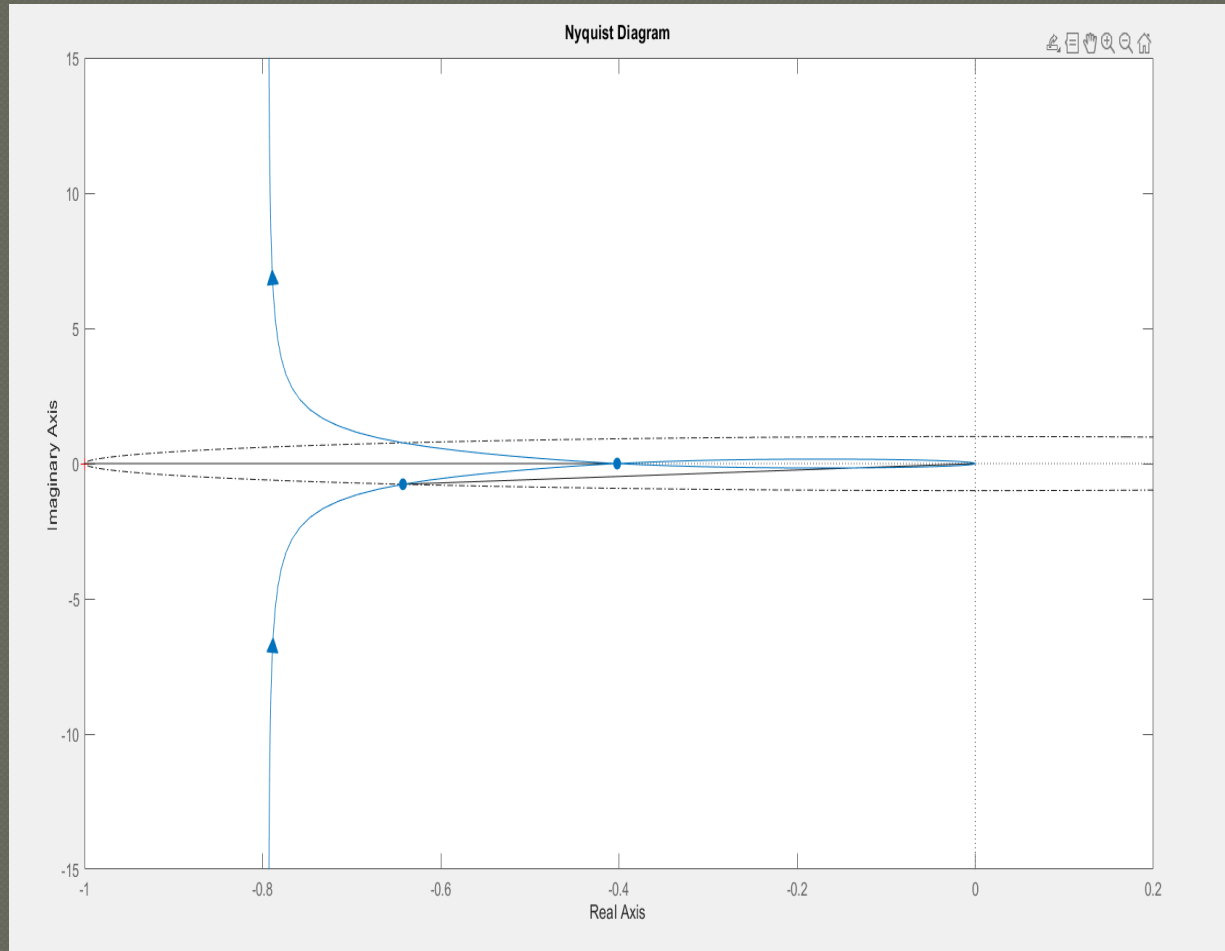


Model Properties

ans =

0
-579.8522
-71.1478

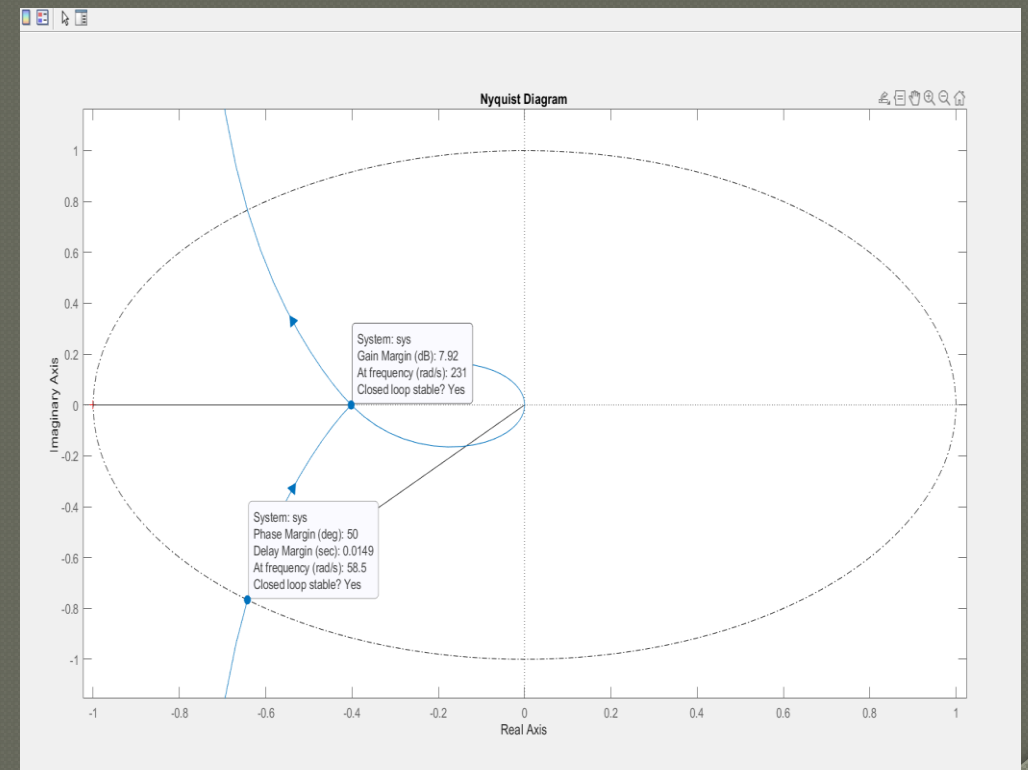

ESR model of Buck-Boost converter:-

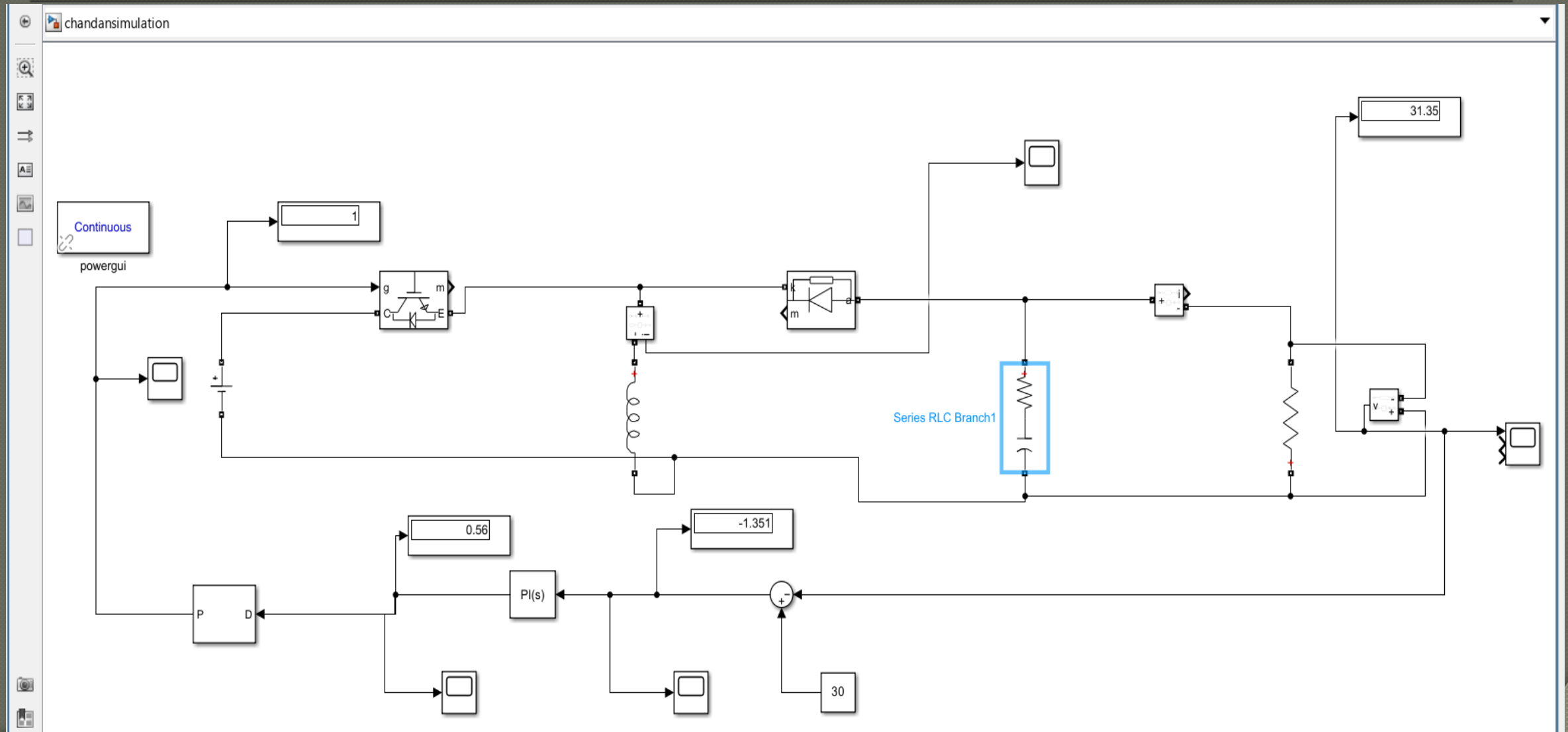

Calculation for ESR :-


→ As we know the small signal model for ESR model

$$\frac{V_o}{d} = \frac{V_{in}}{(1-D)^2} \left(1 - \frac{SDL}{R(1-D)^2} \right) (1 + s\tau_c) \frac{\frac{LC}{(1-D)^2} \left[s^2 + \frac{s}{RC} + \frac{\tau}{L} (1-D)^2 \right] + \frac{(1-D)^2}{LC}}$$

here $L = 10 \times 10^{-3}$
 $C = 480 \times 10^{-6}$
 $D = 0.55$
 $V_{in} = 14 \text{ Volt}$
 $R = 3.2 \Omega$

→ when we use PI controller.
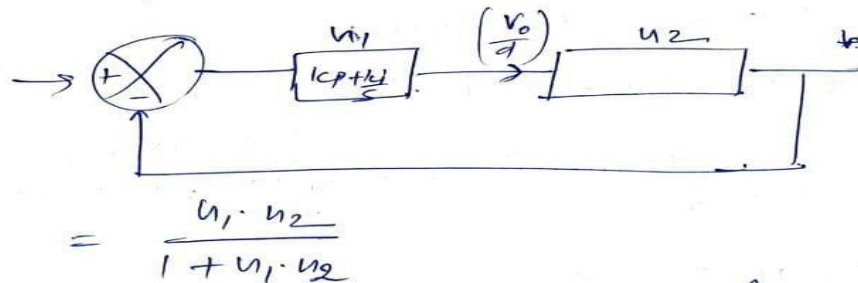
$$\frac{V_{in}}{(1-D)^2} \left(1 - \frac{SDL}{R(1-D)^2} \right) (1 + s\tau_c) \left(K_p + \frac{K_i}{s} \right) \frac{\frac{LC}{(1-D)^2} \left[s^2 + \frac{s}{RC} + \frac{\tau}{L} (1-D)^2 \right] + \frac{(1-D)^2}{LC}}$$



→ In Root locus we draw for OLTF, from which we know

Calculation of ESR:-(continued)

$$\frac{V_{in}}{(1-D)^2} = 69.1358$$

$$\frac{LC}{(1-D)^2} = 23.704 \times 10^{-6}$$

$$k_p = 0.005$$

$$k_i = 0.471$$

$$1 + \frac{69.1358 \left(1 - \frac{5 \times 0.55 \times 10 \times 10^{-3}}{3.2 \times (1 - 0.55)^2}\right) \left(1 + \frac{5 \times 480 \times 10^{-6}}{10 \times 10^{-3}}\right)}{(0.005 + 0.471)}$$

$$+ \frac{23.704 \times 10^{-6} \left[\frac{s^2 + \frac{s}{3.2 \times 480 \times 10^{-6}} + \frac{2(1-0.55)^2}{10 \times 10^{-3}} \right]}{\frac{1}{23.704 \times 10^{-6}}}$$

$$\downarrow 42186.97$$

$$1 + \frac{69.1358 \left(1 - \frac{5 \times 0.55 \times 10 \times 10^{-3}}{3.2 \times (1 - 0.55)^2}\right) \left(1 + \frac{5 \times 480 \times 10^{-6}}{10 \times 10^{-3}}\right)}{(0.005 + 0.471)}$$

$$+ \frac{s^2 (23.704 \times 10^{-6}) + s^2 \times \frac{23.704 \times 10^{-6}}{3.2 \times 480 \times 10^{-6}}}{\frac{1}{23.704 \times 10^{-6}}}$$

$$+ \frac{5 \times 0.55 \times (1 - 0.55)^2}{10 \times 10^{-3}} \times 23.704 \times 10^{-6} + 42186.97$$

$$\frac{1}{23.704 \times 10^{-6}}$$

Calculation of ESR:-(continued)

$$1 + \frac{s(1155s^3 - 27279s^2 - 1.321 \times 10^7 s)}{19440s^3 + 1.025 \times 10^7 s^2 + 3.46 \times 10^{13} s + 2.671 \times 10^{10}}$$

→ Now Root of

$$\frac{s(1155s^3 - 27279s^2 - 1.321 \times 10^7 s)}{19440s^3 + 1.025 \times 10^7 s^2 + 3.461 \times 10^{13} s + 2.671 \times 10^{10}}$$

→ Pole (three poles)

(a) $1.0 \times 10^4 (-0.0264 + 4.2187i)$

(b) $1 \times 10^4 (-0.0264 - 4.2187i)$

~~1×10^4~~

(c) 0

→ three zeros

(a) 0


(b) 119.4137

(c) -95.7955



Varying ESR value:-

```
tf_r =  
  
      1155 s^3 - 27279 s^2 - 1.321e07 s  
-----  
19440 s^3 + 1.025e07 s^2 + 3.46e13 s + 2.671e10  
  
Continuous-time transfer function.  
Model Properties  
  
ans =  
  
      1.0e+04 *  
  
      -0.0264 + 4.2187i  
      -0.0264 - 4.2187i  
      -0.0000 + 0.0000i  
  
ans =  
  
           0  
      119.4137  
     -95.7955  
  
>> |
```



Bode plot with ESR:-

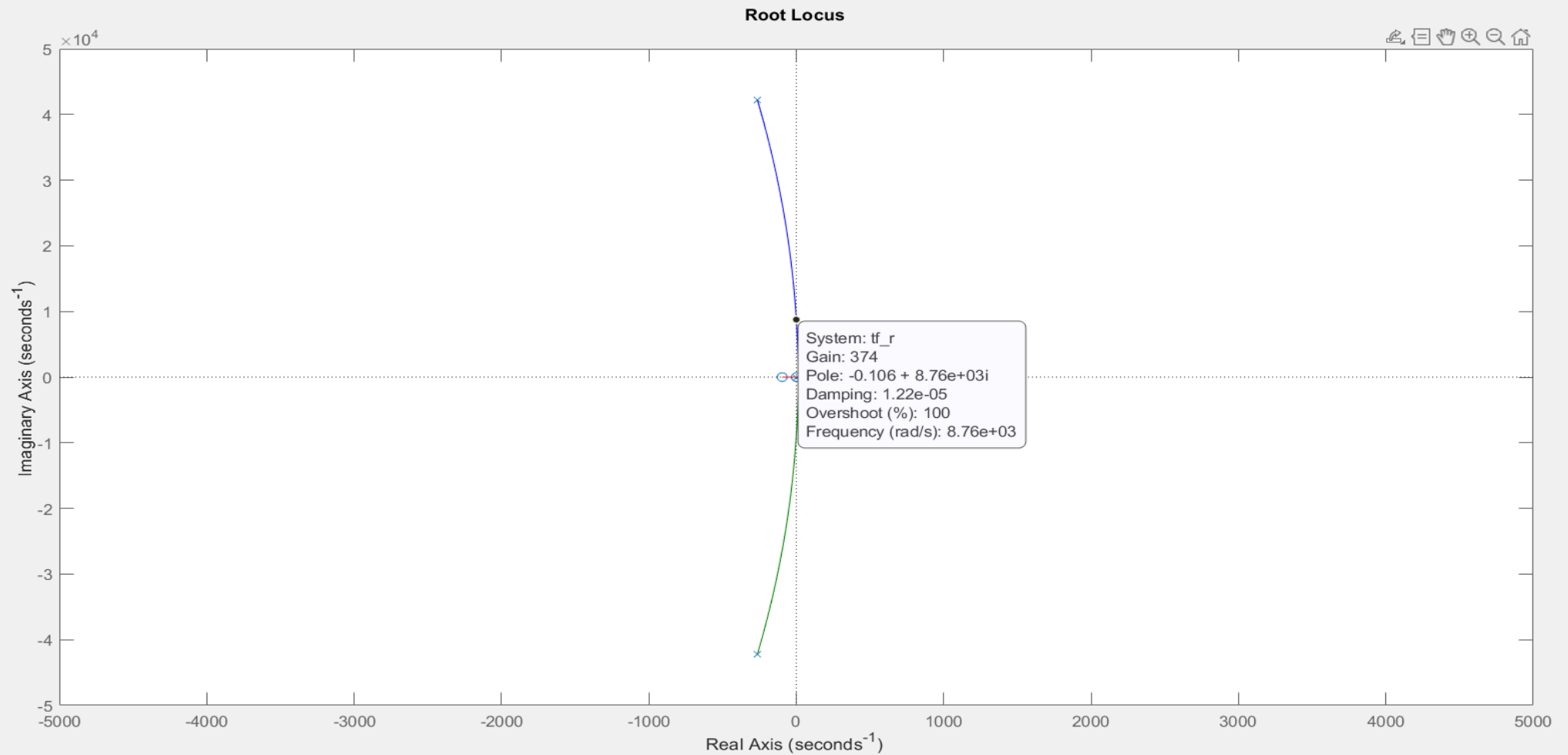

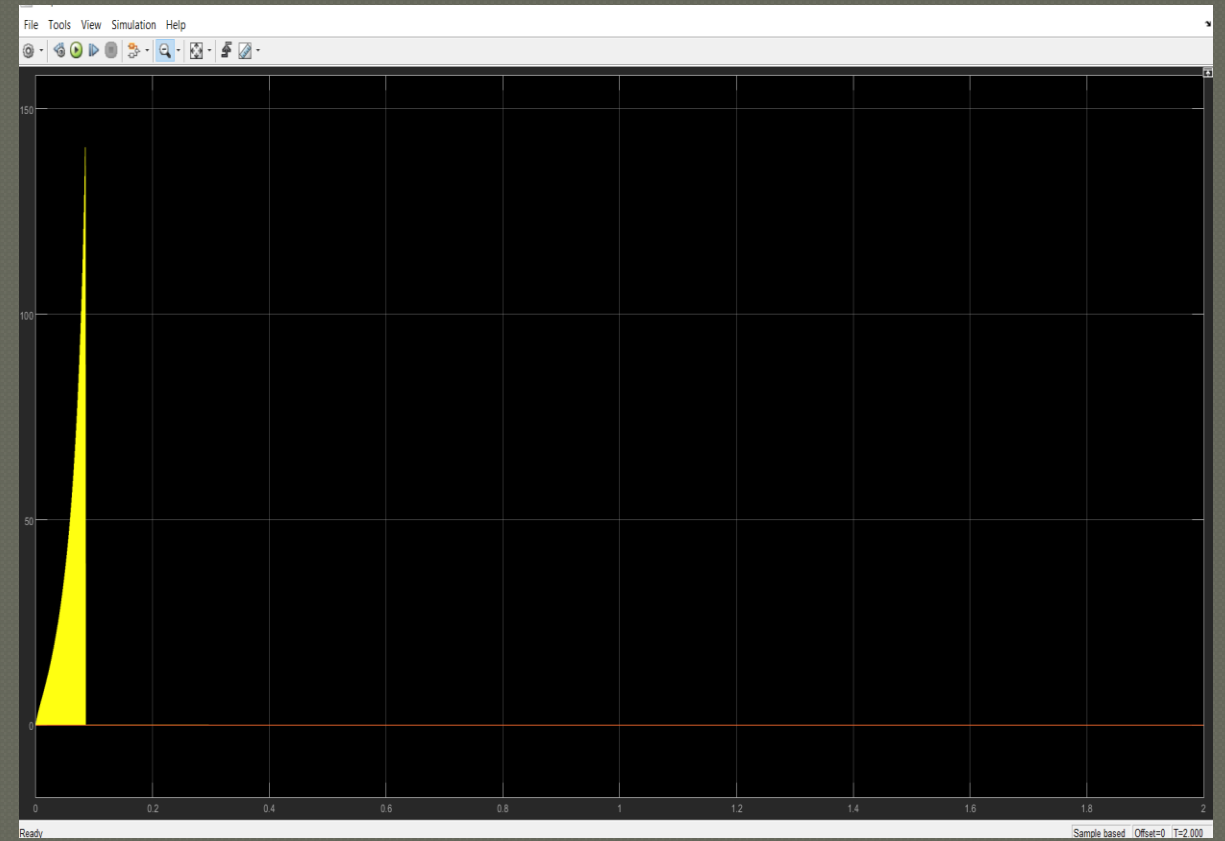
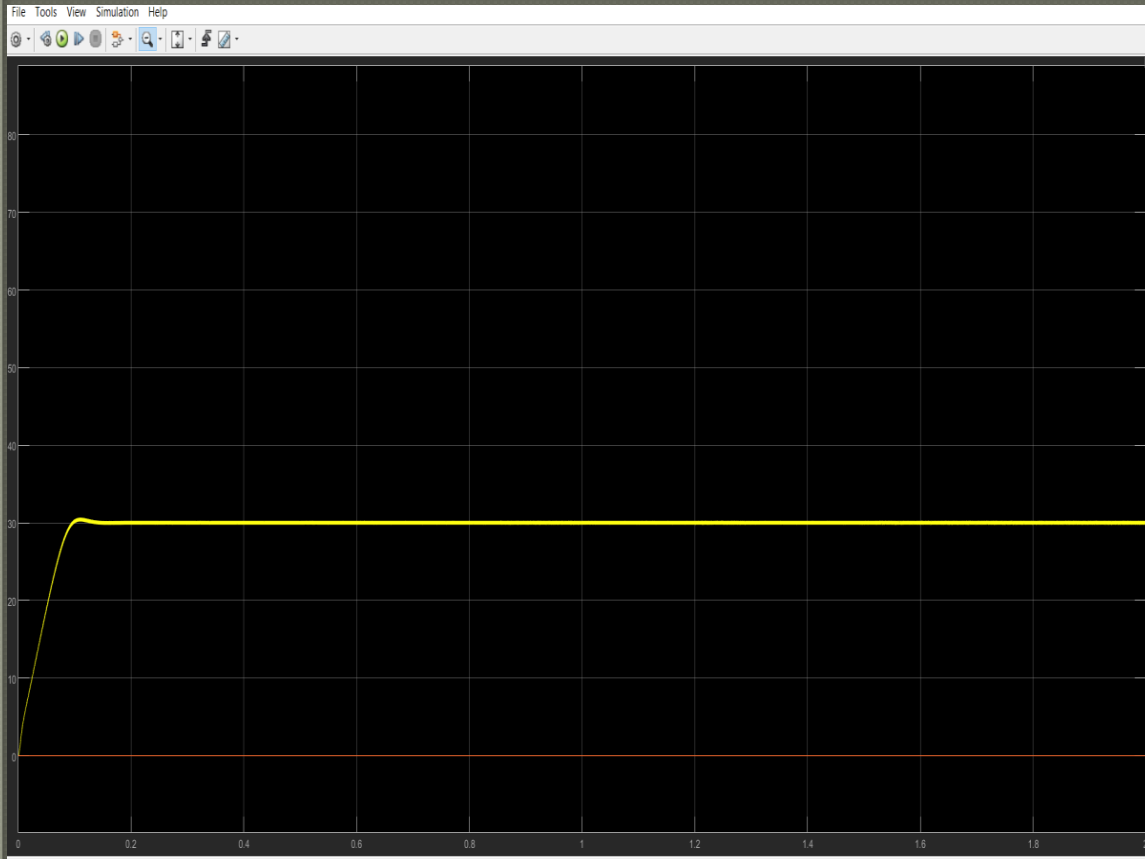
Plot for different value of ESR value(eg:0.1 ohm and 400 ohm):-



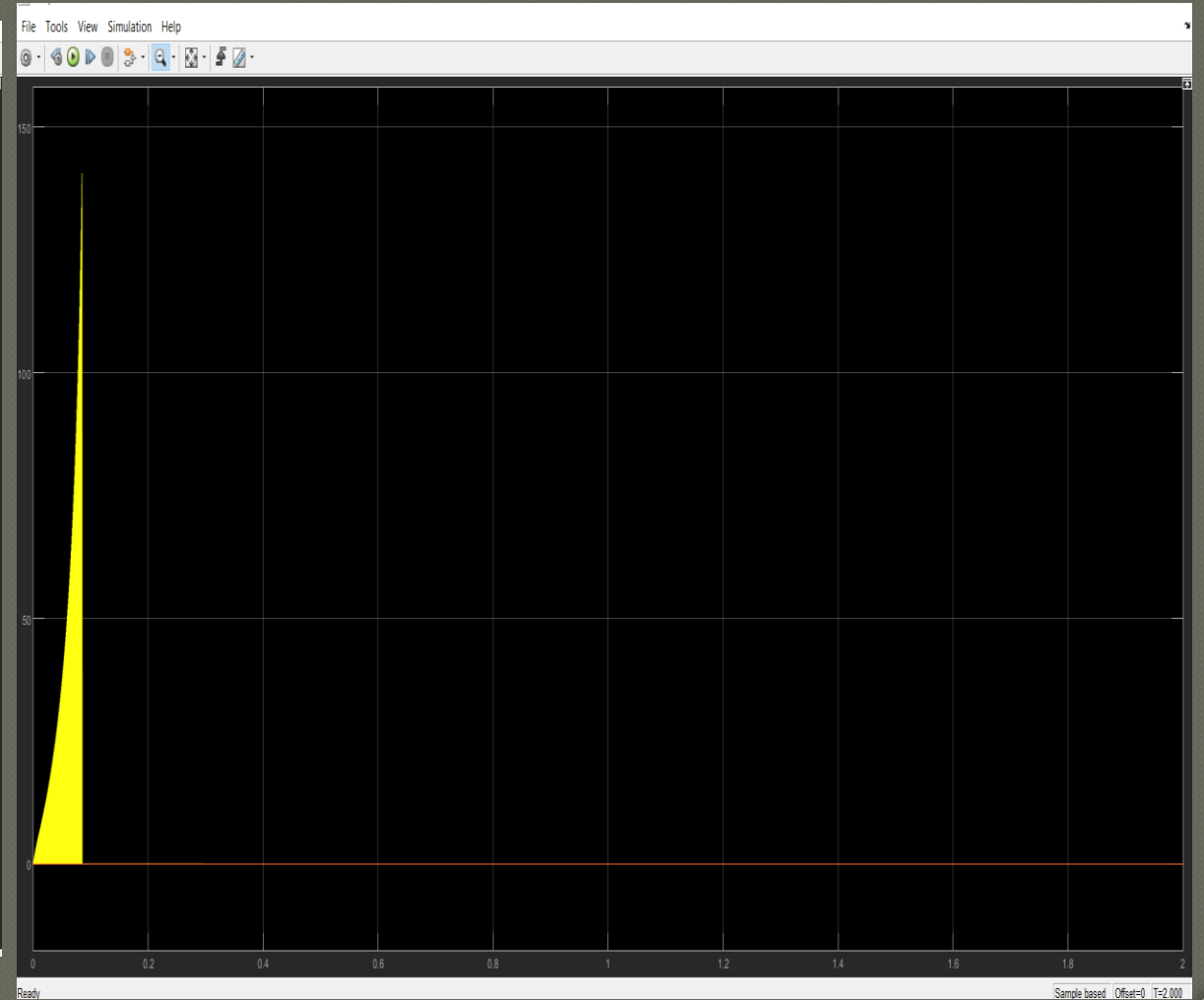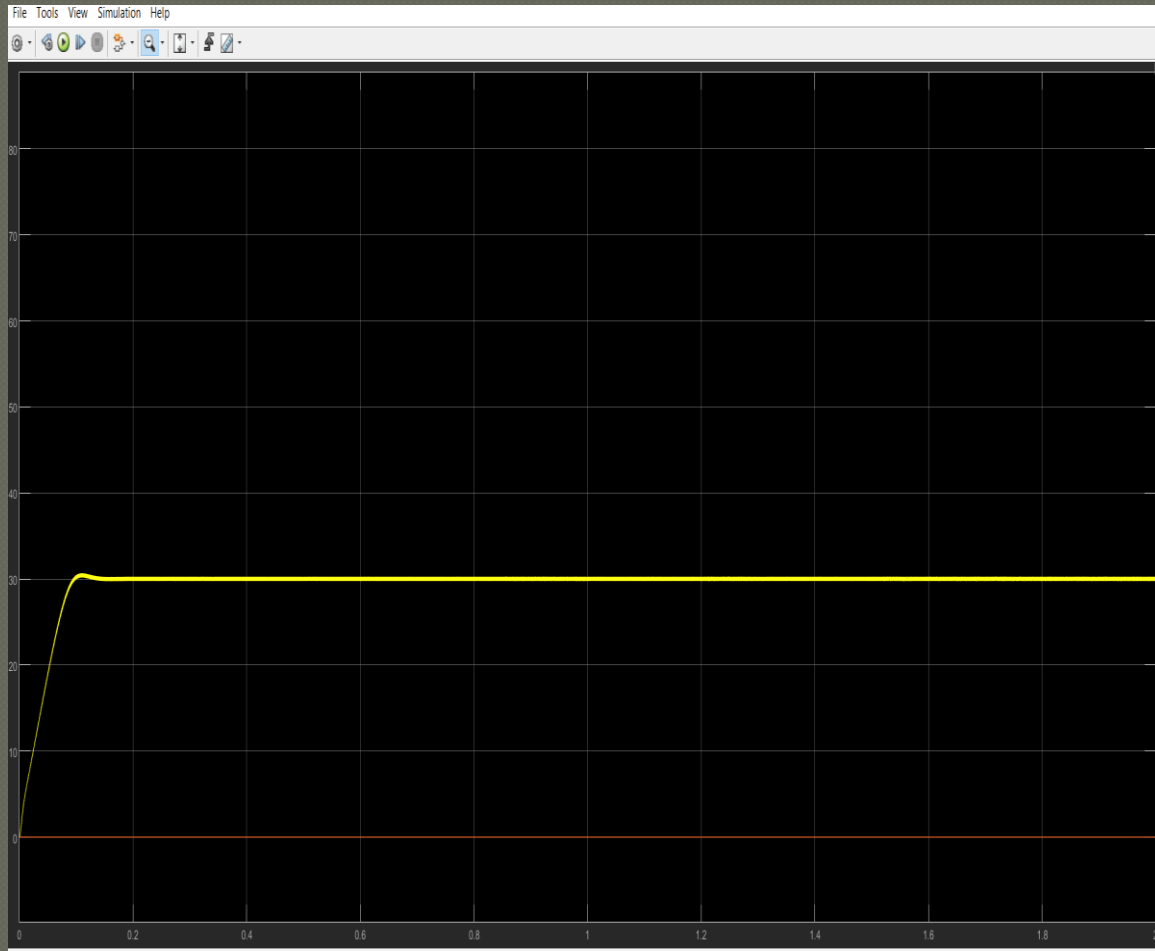Graphs at different ESR value of 0.1 ohm and 400 ohm:-



Observations:-

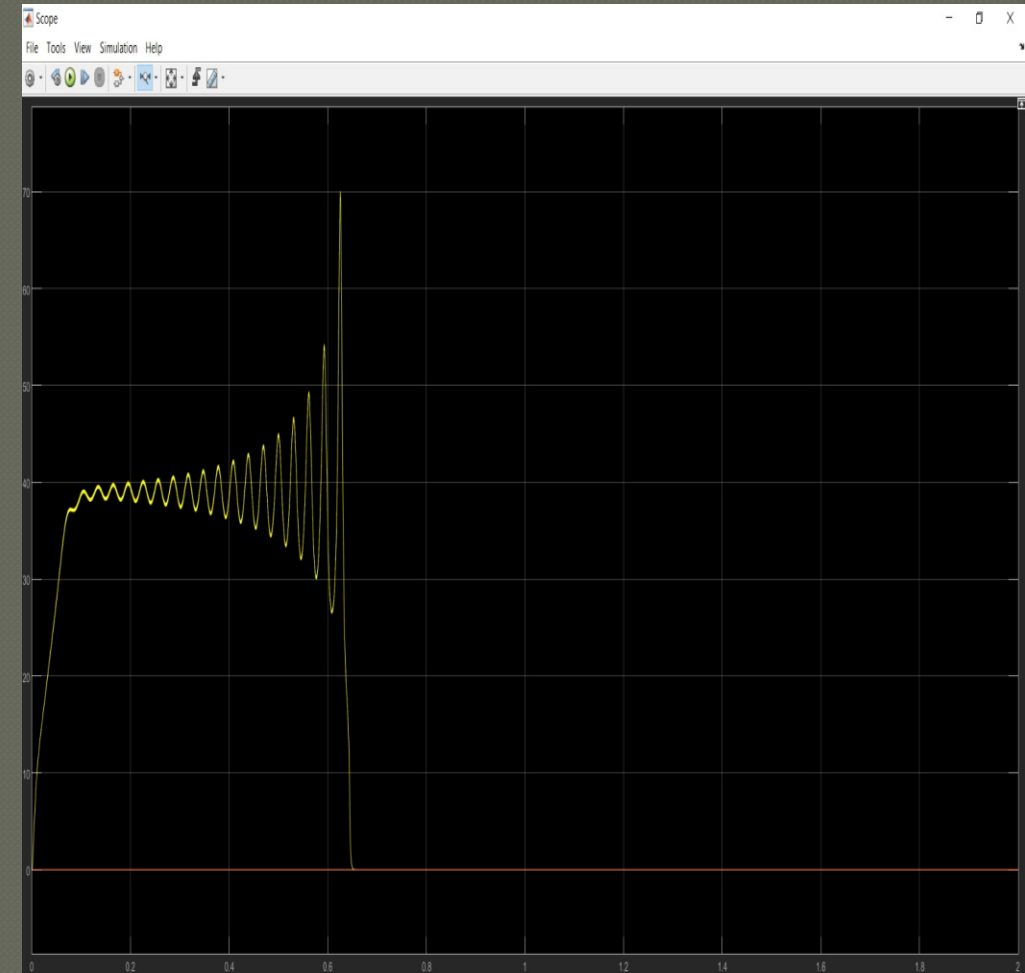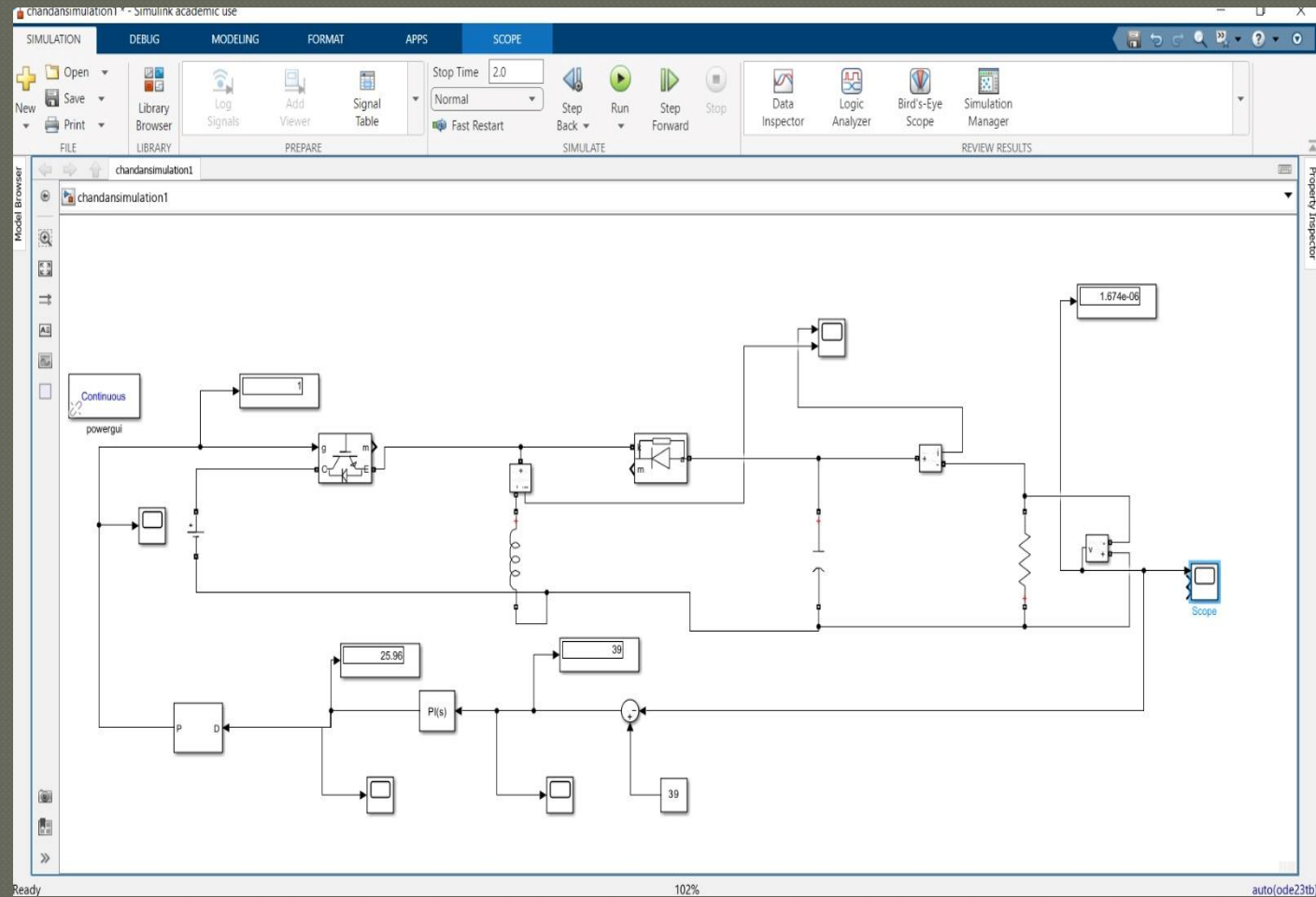

IEEE Reference:-

- Sliding mode control of PV powered DC/DC Buck-Boost converter with digital signal processor

M. E. Şahin, H. İ. Okumuş and H. Kahveci, "Sliding mode control of PV powered DC/DC Buck-Boost converter with digital signal processor," 2015 17th European Conference on Power Electronics and Applications (EPE'15 ECCE-Europe), Geneva, Switzerland, 2015, pp. 1-8, doi: 10.1109/EPE.2015.7309361.

Thank you