

2 STAGE COCKROFT WALTON CIRCUIT (WITH RL LOAD)


SUBMITTED BY:
AMIT KUMAR
(2023EEM1039)
POWER ENGINEERING




SUBMITTED TO:-
PROF. C.C REDDY
(HOD, EED)



TWO STAGE COCKROFT :

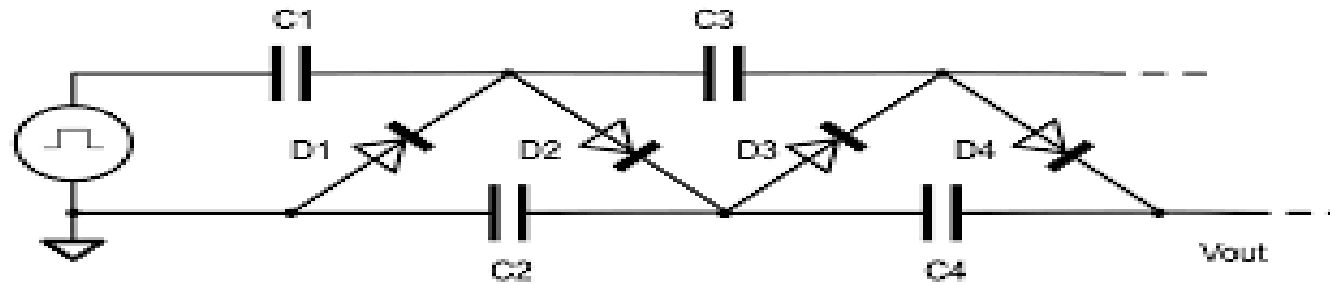


WORKING DIAGRAM:-

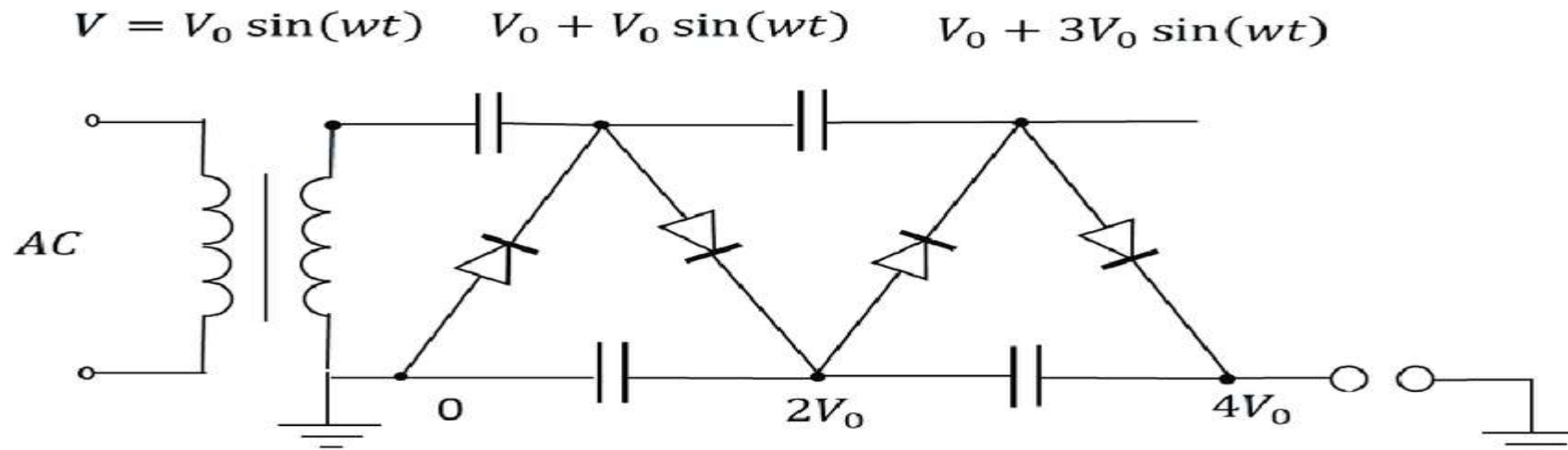


RATING OF ELEMENTS USED IN CIRCUIT:-

- 1) CAPACITOR 22 μ F, 63 V
- 2) DIODE: 1N4007
- 3) RESISTOR: 56k Ω
- 4) INDUCTOR : 330 μ H
- 5) TRANSFORMER: 15-0-15 V


► SIMULATION DIAGRAM

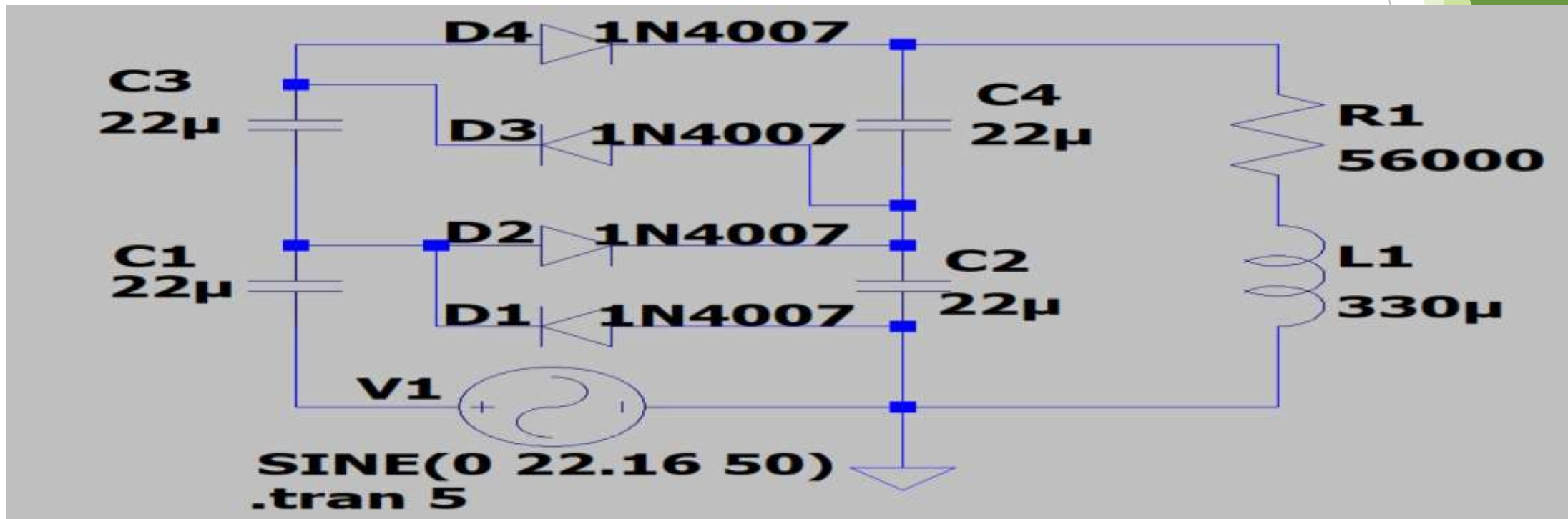

SIMULATION RESULTS:-

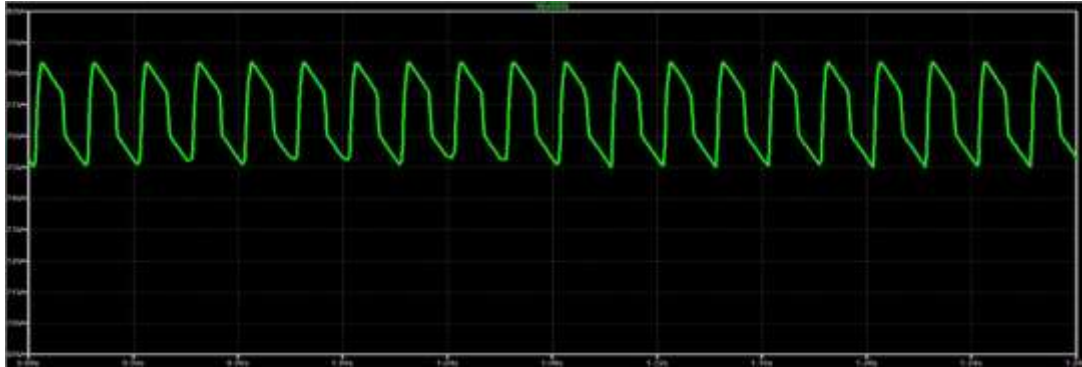


OUTPUT VOLTAGE WAVEFORM

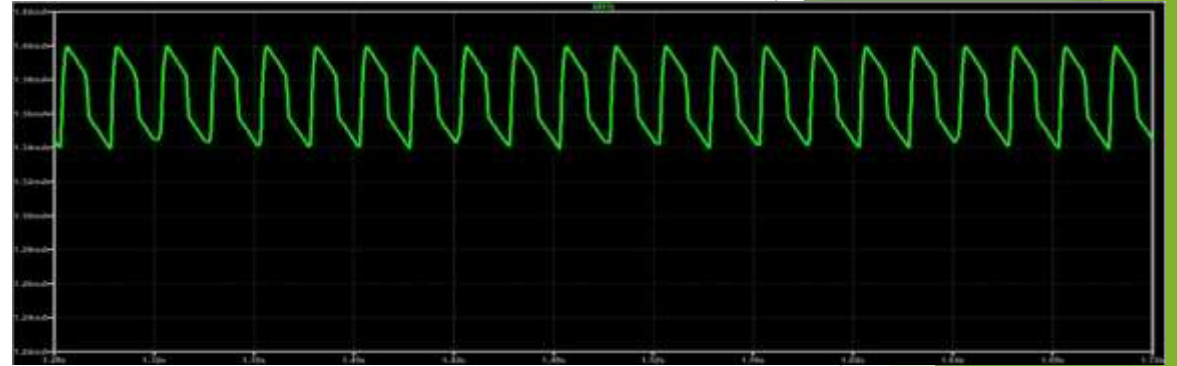


OUTPUT CURRENT WAVEFORM

HARDWARE IMPELNTATION:-

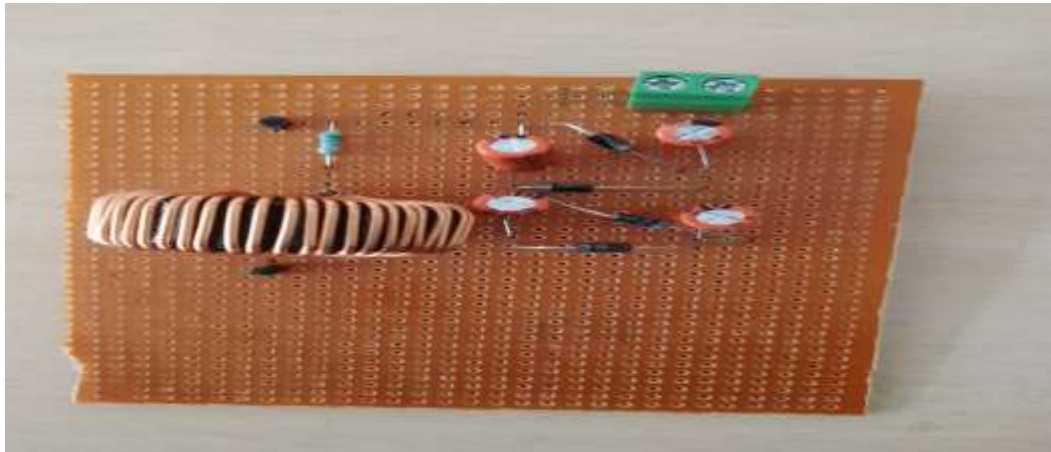

HARDWARE MODEL

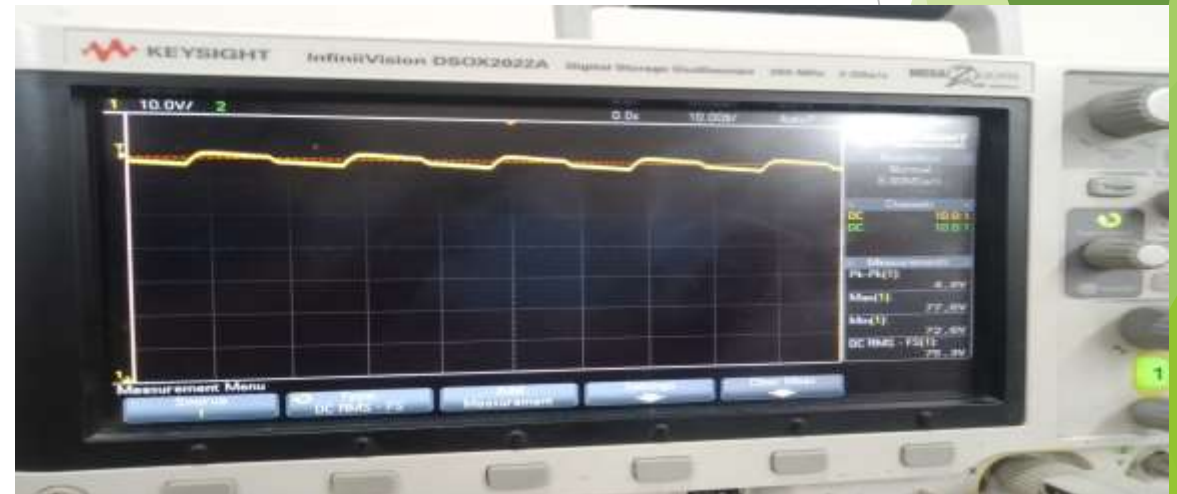

OUTPUT VOLTAGE (HARDWARE)

CALCULATION

- ▶ INPUT VOLTAGE= 15.67 VOLT
- ▶ Impedance=56000.1869 ohm
- ▶ RIPPLE=4.8
- ▶ CURRENT = 1.344 mA
- ▶ $CURRENT = RIPPLE * 2 * f * C = 0.01056 \text{ AMP}$
- ▶ Reduction in Voltage = $(I/fC) * (2n^3/3 + n^2/2 - n/6) = 8.71$
- ▶ Output voltage = $2nVm - \Delta Vm = 79.53$
- ▶ Ripple factor = $\partial V / V_{mean} = 0.060$